

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{V_{in}}{RC}, \quad \text{where } V_{in} = A_0 \cos \omega t$$

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{A_0 \cos \omega t}{RC}$$

Solution has the form

$$\begin{aligned} V &= V_{tr} + V_{ss} \\ &= V_H + V_P \end{aligned}$$

Homogeneous (Transient)

Set  $f(t) = 0$  so

$$\frac{dV_H}{dt} + \frac{V_H}{RC} = 0$$

Solve using separation of variables

Show all steps!

You should get  $V_H = \underset{\substack{\uparrow \\ \text{arbitrary} \\ \text{constant}}}{K} e^{-t/RC}$

Don't solve for  $K$  yet!

Particular (Steady-state)

$$\frac{dV_P}{dt} + \frac{V_P}{RC} = \frac{A_0 \cos \omega t}{RC}$$

$$\frac{d}{dt} + \frac{1}{RC} = \frac{1}{RC}$$

Assume  $V_p$  has a solution of the form

$$V_p = A \sin \omega t + B \cos \omega t$$

Need to find  $A$  &  $B$ .

Find  $\frac{dV_p}{dt} = ?$

Plug  $V_p$  and  $\frac{dV_p}{dt}$  into the ODE

$$\frac{dV_p}{dt} + \frac{V_p}{RC} = \frac{A_0 \cos \omega t}{RC}$$

Multiply both sides by  $RC$

Now do some algebra

Treat the left and right hand sides separately

Get into this form:

$$\begin{aligned} & \underbrace{(\sin \text{ coeffs})}_{\text{sin coeffs}} \sin \omega t + \underbrace{(\cos \text{ coeffs})}_{\text{cos coeffs}} \cos \omega t \\ & = \underbrace{0 \sin \omega t}_{\text{0 sin}} + \underbrace{A_0 \cos \omega t}_{\text{A}_0 \cos} \end{aligned}$$

$$(\sin \text{ coeffs}) = 0$$

$$(\cos \text{ coeffs}) = A_0$$

Solve for  $A$  and  $B$  using these equations

After solving for  $A$  and  $B$ , plug  $A$  and  $B$  into  $V_p$

After solving for A and B, plug A and B into  $V_p$

Lastly solve for K using the full solution and I.C.

$$V = V_H + V_P$$

$$V = K e^{-t/RC} + A \sin \omega t + B \cos \omega t$$

Plug in for A and B

Apply I.C., solve for K

Write full solution using the K you found.